

Type of Document Technical Report	Document ID EPFL-PEL – EE-365 Report 2	Status Final Version
	Author(s) Name(s) Andrea Diez Leboffe 345522 Rodrigue de Guerre 327683	Function BSc Student(s)
	Assistant Name Israel Yepez López, Gaia Petrillo, Celia Hermoso Díaz	Date of Submission 05.04.2024
Title R2: LLC CONVERTER – TRANSFORMER DESIGN		
Course Name EE-365 Power Electronics		
Keywords LLC Converter, Transformer Design, Inductor Design		

TABLE OF CONTENTS

Design Specifications and Constraints	3
Q1: Maximal value for the peak flux density	3
Q2: Estimation of Loss Coefficient	3
Q3: Calculation of Volt-second stress	4
Q4: Calculation of total current stress	4
Q5: Estimation of the window utilization factor	4
Q6: Estimation of losses budget	4
Q7: Target current density	4
Core selection with Kg method	5
Q8: Minimum K_{gfe}	5
Q9: Choice of core from the table of selected materials	6
Q10: Check on the flux density	6
Q11: Calculation of needed Number of Turns according to K_{gfe}	6
Wire Selection	6
Q12: Skin depth	7
Q13: Calculation of fraction of window area to allocate to every winding	7
Q14: Calculation of maximum wire area	7
Q15: Calculation of needed Conductor Area	8
Q16: Wire selection	8
Calculation of Air Gap Length	8
Q17: Air Gap Calculation	8
Q18: Air Gap manufacturability	9
Adjustments considering the Fringing Flux	9
Q19: Fringing flux factor	9
Q20: Adjustment of number of turns due to fringing flux	9
Q21: Check on maximum flux	10
Q22: Evaluation of expected magnetizing inductance value	10
Verification of the Design Constraints and evaluation of Losses	10
Q23: Window utilization factor	10
Q24: DC winding resistance	11
Q25: AC winding resistance	11
Q26: DC e AC copper losses	11
Q27: Estimation of core losses	12
Q28: Thermal consideration	12

Transformer Design summary	12
Q29: LLC transformer design	12
Q30: Overall efficiency of the LLC converter	13
Transformer Building Procedure	14
Q31: Wiring of the transformer	14
Q32: Air gap and assembly of the transformer	14
Q33: Verifying the wiring directions	15
Q34: Soldering	15
Transformer Measuring Procedure	17
Q35: Open Circuit test with RLC meter	17
Q36: Short Circuit test with RLC meter	17
Q37: Open Circuit test with Bode 100 meter	18
Q38: Short Circuit test with Bode 100 meter	19
Q39: Saturation measurements	20
Q40: Magnetizing current and Voltage Ratio check	22
Q41: Heat-run test	23
Design of the resonant inductor	24
Q42: Evaluate the external inductance	24
Q43: Design of the external inductance	24
Q44: Check for B value of your inductor	24
Q45: Winding and measurement of the inductor	25
Q46: Check expected copper losses in the inductor	25

DESIGN SPECIFICATIONS AND CONSTRAINTS

The second part of the project deals with the design and realization of the magnetic components (i.e. the transformer and the resonant inductor), according to specifications and requirements from Part 1. Fill out Table 1 with the parameters assigned to your group and calculated in the previous Report. Since, for all the groups, the range of the converter's operating frequencies can vary from 50 kHz to 400 kHz, ferrite was chosen as a core material. Thereby, the N87 ferrite material (datasheet pdf) is considered.

Be aware that you need to design the transformer so that its magnetizing inductance matches the L_m needed for your LLC Converter. You are not required to match the leakage inductance of the transformer to your L_r since it will be possible to add an additional external inductor to obtain the needed value. Therefore, the suggested design drives are: matching the needed value of L_m with the magnetizing inductance, and obtaining a leakage inductance lower or equal than the desired L_r (it will be possible to add external inductance to increase the total inductance value to match the desired one, while it will not be possible to decrease it).

To successfully complete the second part of the project, it is essential to go through the corresponding lecture slides before starting to work on the report. To provide your answers and explanations, use the framed boxes below each question. For the questions where no box for explanations is provided, it is sufficient to only write the solution to the question, without providing any additional reasoning. Consider that this design process is iterative and you will need to go back and rethink your previous decisions whenever you will find out that some constraints are broken or that they lead to unfeasible or undesired operating conditions. You do not need to report every iteration nor give written track of all the iterations. Report only your final design choices and take care of checking that they comply to all the constraints given in the previous and following steps.

Table 1 Given parameters and design requirements for the LLC converter transformer and resonant inductor. *Note:* While filling the table consider the different operating condition analyzed in Report 1 and only include here the highest value for current peak and rms values.

Property	Value	Unit
f_{res}	160	kHz
f_{min}	115.25	kHz
V_{max}	50	V
V_{min}	40	V
P_{out}	50	W
$I_{Lr,peak}$	7.45	A
$I_{Lr,rms}$	3.05	A
$I_{Dr,rms}$	1.97	A
n	1.04	-
L_m	18.25	μ H
L_r	3.65	μ H
ΔT_{goal}	< 50	K

Q1: MAXIMAL VALUE FOR THE PEAK FLUX DENSITY

To avoid core saturation, the target peak flux density must be constrained to a value well below the saturation flux density value of the core material. The magnetization curves of the available core materials N87 datasheet. Constrain the maximal value of the peak flux density $B_{pk,max}$ well below the saturation flux density value of these core materials. This is a trade-off between the use of the core and core losses.

$$B_{pk,max} = 320 \text{ mT}$$

/ 2 pt.

Q2: ESTIMATION OF LOSS COEFFICIENT

To estimate core loss coefficient is possible to use empirical formula derived from Steinmetz equation and given in Equation 1. For the selected material you can use $a = 1.5$ and density $D = 0.00485 \text{ kg/cm}^3$. Notice that the losses depend of frequency and that the design should consider the worst case. Reflect on which operating frequency would represent the worst case for core losses and calculate the worst case loss coefficient using the given formula

$$K_{fe} = 0.262 \cdot 10^{-3} \cdot f^a \cdot D \tag{1}$$

$$f_{worst-case} = 160 \text{ KHz}$$

$$K_{fe} = 81.3248 \text{ W/T}^b \text{ cm}^3$$

/ 2 pt.

Q3: CALCULATION OF VOLT-SECOND STRESS

Volt-second stress is the integral of the primary voltage waveform over the positive half cycle. You can assume primary voltage in the positive half cycle to be equal to input voltage (constant). Evaluate the volt-second stress in different operating conditions (e.g. $V_{\min} - f_{\min}$ and $V_{\max} - f_{\text{res}}$) and report here the worst case condition (the highest value).

$$V_{\min} - f_{\min} \Rightarrow \lambda = \frac{40}{2} \cdot \frac{1}{115.25 \cdot 10^3} = 1.735 \cdot 10^{-4} \text{ V-sec}$$

and

$$V_{\max} - f_{\text{res}} \Rightarrow \lambda = \frac{50}{2} \cdot \frac{1}{160 \cdot 10^3} = 1.563 \cdot 10^{-4} \text{ V-sec}$$

$$\lambda = 1.735 \cdot 10^{-4} \text{ V-sec}$$

/ 2 pt.

Q4: CALCULATION OF TOTAL CURRENT STRESS

As explained in the slides, calculate your total current stress. Be aware that your transformer is composed by three windings, I_{Lr} is your primary current and I_D is the current in each of your secondaries.

$$I_{\text{tot}} = 7.15 \text{ A}$$

/ 1 pt.

Q5: ESTIMATION OF THE WINDOW UTILIZATION FACTOR

The core window area is besides the winding, also consumed by non-conductive materials. Make an estimation of the window utilization factor K_u , also known as the fill factor, to start your design. Be aware that this is only a first estimate and a reference value for yourself, throughout the process and once the core sample is wound you will be able to improve this estimate for the next design iteration.

$$K_u = 0.6$$

/ 1 pt.

Q6: ESTIMATION OF LOSSES BUDGET

Set a reasonable target efficiency for your design and calculate your allowed losses P_{tot} considering the nominal output power. Be aware that this is only a first estimate and you will be able to improve it for the next iterations.

We are trying to achieve an efficiency of 95%, which would mean 5% of losses, equivalent to 2.5W of losses

$$P_{\text{tot}} = 2.5 \text{ W}$$

/ 2 pt.

Q7: TARGET CURRENT DENSITY

Unlike lone wires in free-air electric installations and PCB tracks, densely packed multi-layer windings cannot dissipate loss heat just as well with only natural air cooling. It is a trade-off between copper losses respectively temperature rise and power density. Considering the usual values given in the slides, select a certain current density constraint to start your design. While you go through the following steps of the process or once you prototype your first design, you can adjust this constraint and re-iterate your design to optimize it in one of the directions. Note that due to discrete wire gauges it will not be possible to exactly match the selected value.

$$J_w^* = 5 \text{ A/mm}^2$$

/ 1 pt.

CORE SELECTION WITH KG METHOD

As suggested in the slides and in literature one of the most commonly used methods to design a transformer is the K_g method, modified for AC applications to take into account both core and copper losses and to minimize them. This method is usually referred to as K_{gfe} method. (More details can be found in the slides or in the book *Fundamentals of Power Electronics* by Erickson and Maksimovic, Springer)

Magnetic core manufacturers provide a vast variety of core shapes and sizes. In this course, a preselection of suitable cores is given in Table 2. The geometrical K_{gfe} factor for each of the available core is also calculate considering the geometrical dimension given in the databooks and $\beta = 2.7$ as is usually done for ferrites. You are requested to choose one of the available cores for your design.

Table 2 Available core materials and core shapes.

Core shape	N87 core	Coil former	Yoke	$K_{gfe} [cm^5]$
E20/10/6	B66311G0000X187	B66206B1110T001	B66206A2010X000	0.0022
E25/13/7	B66317G0000X187	B66208X1010T001	B66208A2010X000	0.0042
E30/15/7	B66319G0000X187	B66232B1114T001	B66232A2010X000	0.0056
E32/16/9	B66229G0000X187	B66230A1114T001	B66230A2010X000	0.0089
ETD34/17/11	B66361G0000X187	B66362X1014T001	B66362A2000X000	0.0114
ETD39/20/13	B66363G0000X187	B66364B1016T001	B66364A2000X000	0.0200
ETD44/22/15	B66365G0000X187	B66366B1018T001	B66366A2000X000	0.0300

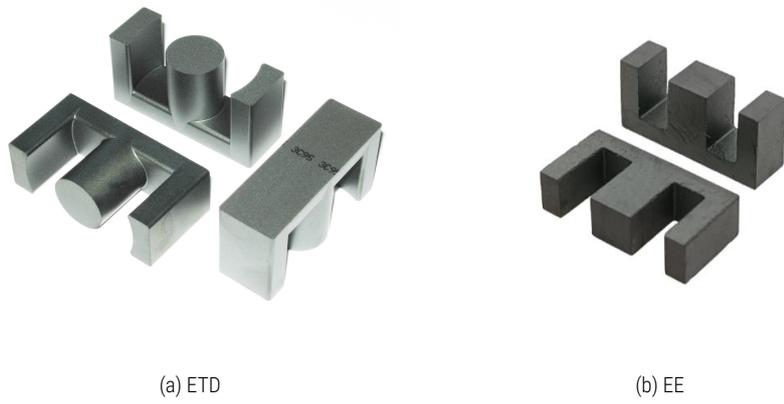


Figure 1 Core shapes

Q8: MINIMUM K_{gfe}

Using the values calculated and estimated in previous section, and considering $\beta = 2.7$, calculate the minimum required K_{gfe} needed in your specific conditions. Copper resistivity can be considered to be $\rho = 1.724 \cdot 10^{-6} \Omega cm$. **Note:** while performing the calculations be careful to use the correct units (e.g. dimensions in cm or cm^2 , currents in A , power in W)

$$K_{gfe} \geq \frac{\rho \lambda^2 I_{tot}^2 K_{fe}^{2/\beta}}{4 K_u P_{tot}^{\frac{\beta+2}{\beta}}} 10^8 = \frac{1.724 \cdot 10^{-6} \cdot (1.735 \cdot 10^{-4})^2 \cdot 7.15^2 \cdot 81.3248^{2/2.7}}{4 \cdot 0.6 \cdot 2.5^{\frac{2.7+2}{2.7}}} \cdot 10^8 = 0.000583 cm^5$$

$$K_{gfe} = 5.834 \cdot 10^{-4} cm^5$$

/ 3 pt.

Q9: CHOICE OF CORE FROM THE TABLE OF SELECTED MATERIALS

Indicate the core shape from Table 2 that you want to use for your design, considering the needed minimum K_{gfe} . As first attempt, you can choose whatever core that has a K_{gfe} bigger than the needed one, bigger cores will reduce the power density of your converter. Be aware that your core size also has an influence on current density and losses. These are going to be analyzed in the following questions. It is very likely that you will need to iterate your answer on this question to meet all the constraints.

Core shape: E25/13/7

/ 3 pt.

Q10: CHECK ON THE FLUX DENSITY

Using the formula presented in the slides, check that the expected ΔB (peak ac flux density, peak-to-average) in your operating conditions is never exceeding the $B_{pk,max}$ selected in Q1. This will ensure that saturation never occurs in the expected operating conditions. Information on the geometrical dimensions of the selected cores can be found in the provided core databook (i.e. Ferroxcube - pdf here)

From the datasheet, we find $A_e = A_c = 52.0mm^2 = 52 \cdot 10^{-2}cm^2$

$$\Delta B = \left[10^8 \cdot \frac{\rho \cdot \lambda_{tot}^2}{2 \cdot K_u} \cdot \frac{MLT}{W_a \cdot A_c^3 \cdot l_m} \cdot \frac{1}{\beta \cdot K_{fe}} \right]^{\frac{1}{\beta+2}}$$

$$= \left[10^8 \cdot \frac{1.724 \cdot 10^{-6} \Omega \cdot cm \cdot (1.735 \cdot 10^{-4} V \cdot sec)^2 \cdot (7.15A)^2}{2 \cdot 0.6} \cdot \frac{4.9cm}{0.56cm^2 \cdot (0.52cm^2)^3 \cdot 5.8cm} \cdot \frac{1}{2.7 \cdot 81.3248W/T^{\beta} cm^3} \right]^{\frac{1}{2.7+2}}$$

$$= 0.08776T = 87.76mT < 320mT = B_{pk,max}$$

Which confirms that the expected ΔB is never exceeding $B_{pk,max}$.

$\Delta B : 87.76mT$

/ 2 pt.

Q11: CALCULATION OF NEEDED NUMBER OF TURNS ACCORDING TO K_{gfe}

Using the formula presented in the slides, calculate the desired number of turns on the primary side to minimize the total losses. Then, considering the transformer ratio required for your design, calculate the number of turns needed for your secondaries. Make sure that each winding is composed by a integer number of turns. **Note:** while performing the calculations be careful to use the correct units (e.g. dimensions in cm or cm^2 , flux density in T)

$$N_1 = \frac{\lambda_1}{2 \cdot \Delta B \cdot A_c} \cdot 10^4 = \frac{1.735 \cdot 10^{-4} V \cdot sec}{2 \cdot 87.76 \cdot 10^{-3} T \cdot 0.52cm^2} \cdot 10^4 = 19. \approx 19$$

$$n = \frac{N_1}{N_2} \Rightarrow N_2 = \frac{N_1}{n} = \frac{19}{1.04} = 18.28 \approx 18$$

$N_1 = 19$

$N_{2,1} = 18$

$N_{2,2} = 18$

$n = 1.04$

/ 3 pt.

WIRE SELECTION

The following step in the transformer design is to select a suitable wire. Different aspects needs to be considered in this choice. Increasing the wire cross section would reduce the resistance, but at the same time would lead to an higher utilization factor or to the need for a bigger core. In addition, operating condition are set in the range 50 – 400kHz, this leads to a significant weight of skin effect on the effective AC resistance. In the following tables, you will find a list of the materials available.

Table 3 Available magnet wires.

Wire number	M1	M2	M3	M4	M5	M6	M7
Conductor diameter [mm]	0.65	0.9	1.0	1.2	1.54	1.6	1.8

Table 4 Available Litz wires (single conductor diameter 0.2mm).

Wire number	L1	L2	L3	L4
Number of strands	25	35	45	80
Total Conductive Area [mm ²]	0.78	1.10	1.41	2.51
External Diameter [mm]	1.53	1.8	2.06	2.8

Q12: SKIN DEPTH

To develop a feeling of the specific weight of skin effect on your design evaluate the skin depth at your minimum and maximum operating frequency.

$$SkinDepth = \delta = \sqrt{\frac{\rho}{\pi f \mu_r \mu_0}}$$

$$\delta_{f,min} = \sqrt{\frac{1.724 \cdot 10^{-6} \Omega \cdot m \cdot 10^{-2}}{\pi \cdot 115.25 \cdot 10^3 Hz \cdot 1 \cdot 4\pi \cdot 10^{-7}}} \cdot 10^3, \quad \delta_{f,max} = \sqrt{\frac{1.724 \cdot 10^{-6} \Omega \cdot m \cdot 10^{-2}}{\pi \cdot 160 \cdot 10^3 Hz \cdot 1 \cdot 4\pi \cdot 10^{-7}}} \cdot 10^3$$

$\delta_{f,min} = 0.195mm$ $\delta_{f,max} = 0.165mm$ / 3 pt.

Q13: CALCULATION OF FRACTION OF WINDOW AREA TO ALLOCATE TO EVERY WINDING

Take into account the rms current expected in each winding, the calculated number of turns and the total current calculated in the first section. Calculate the fraction of window area that should be allocated to each of your three windings.

$$a_1 = \frac{n_1 \cdot I_1}{n_1 \cdot I_{tot}} = 0.427, \quad a_{2,1} = \frac{n_2 \cdot I_2}{n_1 \cdot I_{tot}} = 0.261, \quad a_{2,2} = \frac{n_2 \cdot I_2}{n_1 \cdot I_{tot}} = 0.261$$

$a_1 = 0.427$ $a_{2,1} = 0.261$ $a_{2,2} = 0.261$ / 2 pt.

Q14: CALCULATION OF MAXIMUM WIRE AREA

Considering the dimensions of the selected core and the allocated fraction for each wire winding, calculate the maximum wire area that would fit in the available space. Note that this represent the total conductor area.

$$A_{wi} = \frac{\alpha_i \cdot K_u \cdot W_A}{n_i}, \quad A_{w,max} \leq \frac{1}{n} \cdot W_A \cdot K_u$$

$$A_{w1,max} = \frac{0.427 \cdot 0.6 \cdot 56mm^2}{19}, \quad A_{w21,max} = \frac{0.261 \cdot 0.6 \cdot 56mm^2}{18}, \quad A_{w22,max} = \frac{0.261 \cdot 0.6 \cdot 56mm^2}{18}$$

$A_{w1,max} = 0.755mm^2$ $A_{w21,max} = 0.487mm^2$ $A_{w22,max} = 0.487mm^2$ / 2 pt.

Q15: CALCULATION OF NEEDED CONDUCTOR AREA

Consider your target current density defined in Q7 and the rms current expected in your windings according to simulation performed in Report 1. Evaluate the Total Conductive area (A_{TC}) needed to satisfy your requirement. Compare this area with the maximum available in the core you selected (see the answer form previous question). If the available area (Q14) is smaller than the needed one (Q15), go back to Q9 and select a bigger core. Note that if the needed area is only slightly bigger than the maximum available one, you can choose to proceed with your selected core, although pay special attention to utilization factor control (Q23) to make sure that your design is still feasible. Be aware that core selection will also be influenced by next question answers, consider to reiterate your design taking into account also information and choices taken in Q16.

$$A_{TC,1} = \frac{I_1}{J_w^*} = \frac{3.05A}{5A \cdot mm^{-2}} \quad , \quad A_{TC,2} = \frac{I_{2,1}}{J_w^*} = \frac{1.97}{5A \cdot mm^{-2}} \quad , \quad A_{TC,3} = \frac{I_{2,2}}{J_w^*} = \frac{1.97}{5A \cdot mm^{-2}}$$

$A_{TC,1} = 0.61mm^2$ $A_{TC,2} = 0.394mm^2$ $A_{TC,3} = 0.394mm^2$ / 3 pt.

Q16: WIRE SELECTION

Now consider the available wires in Table 3 and 4. For Magnet Wires (Table 3) you can consider Total Conductive area as the total area of the wire, for Litz Wires (Table 4) the total conductive area is given in the Table. Once again consider target current density (Q7) and expected rms current (Report 1), in addition use expected needed total conductor area (Q15) as a guideline. Select the wire that is most suitable for your case. Note that due to the limited number of wire choices available you may not be able to realize exactly your target current density, choose the closest possible value considering the wire technology of your choice. Check that the area needed for your selected winding is lower than the maximum available one (Q14), otherwise reconsider your core choice (Q9). Note that your technology choice (Magnet or Litz wire) will effect your losses and the size of your transformer, you may want to reconsider your choice after calculating AC losses in Q25. In your reply, indicate the label given in the table to the wire of your choice.

For the first wire (1) we want an area in between $[0.61mm^2, 0.755mm^2]$. The M2 wire has an area of $\pi \cdot (\frac{0.9mm}{2})^2 = 0.636mm^2$ which fits in our requirements.
 For the second wire (2,1 2,2) we need an area between $[0.394mm^2, 0.487mm^2]$. The M1 wire has an area of $\pi \cdot (\frac{0.65mm}{2})^2 = 0.332mm^2$, which is not exactly in our targeted range but close enough. Indeed with this wire, instead of the targeted current density $J_w^* = 5A/mm^2$, we should get a current density of $J_w^* = \frac{I_2}{A_{TC,w2}} = \frac{1.97A}{0.332mm^2} = 5.934A/mm^2$ which is just below the maximum one.

Selected wire 1: M2 $A_{w1,selected} = 0.636mm^2$ $A_{TC,1,sel} = 0.61mm^2$ $J_{w1,selected} = 4.795A/mm^2$
 Selected wire 2,1: M1 $A_{w21,selected} = 0.332mm^2$ $A_{TC,21,sel} = 0.332mm^2$ $J_{w21,result} = 5.934A/mm^2$
 Selected wire 2,2: M1 $A_{w22,selected} = 0.332mm^2$ $A_{TC,22,sel} = 0.332mm^2$ $J_{w22,selected} = 5.934A/mm^2$ / 4 pt.

CALCULATION OF AIR GAP LENGTH

Q17: AIR GAP CALCULATION

As defined in the introduction of this report, your objective is to design the magnetizing inductance of your transformer to match the needed magnetizing inductance for your design. The magnetizing inductance is depending on the number of turns and on the reluctance of the magnetic path. Once the number of turns, the material and the core shape have been fixed, one degree of freedom is left

in the air gap length. Calculate the total air gap needed in your design and provide your reasoning.

$$l_{g,tot} = R_g \cdot \mu_0 \cdot A_c = \frac{N^2 \cdot \mu_0 \cdot A_c}{L_m} = \frac{19 \cdot 4\pi \cdot 10^{-7} \text{H/m} \cdot 0.52 \cdot 10^{-4} \text{m}^2}{18.25 \cdot 10^{-6} \text{H}} \cdot 10^3$$

$$l_{g,tot} = 1.29 \text{mm}$$

/ 4 pt.

Q18: AIR GAP MANUFACTURABILITY

To ensure easy manufacturability, the air gap will be realized inserting certain number of layers of Kapton tape (thickness of one layer $65\mu\text{m}$). Remember that the gap will be inevitably present two times in the magnetic path (tape will be placed in the two external legs of the core), therefore adjust the needed value and calculate the number of Kapton tape needed for each side. Consider that only an integer number of layers can be chosen, calculate the total manufactured gap.

$$\text{number of layers} = \frac{1}{2} \cdot \frac{l_{g,tot}}{65 \cdot 10^{-3}} = \frac{1}{2} \cdot \frac{1.29 \text{mm}}{65 \cdot 10^{-3}} \approx 9, \quad l_{g,tot,real} = \text{number of layers} \cdot 65 \cdot 10^{-3} = 9 \cdot 65 \cdot 10^{-3}$$

$$\text{Number of needed Kapton layers per side} = 9$$

$$l_{g,tot,real} = 0.585 \text{mm}$$

/ 3 pt.

ADJUSTMENTS CONSIDERING THE FRINGING FLUX

Q19: FRINGING FLUX FACTOR

Due to the introduction of the air gap, it is not possible to consider an ideal magnetic flux distribution, but it is essential to consider that magnetic flux spreads out into the surrounding medium, in proximity of the air gap. This effect modifies the magnetizing inductance value. Calculate the fringing flux factor F_{fringe} . Use the winding width value G from the coil former data sheet (Nominal Winding Width in Ferroxcube databook).

From the datasheet, we get $G = 15.45 \text{ mm}$. We then find:

$$F_{\text{fringe}} = 1 + \frac{l_{g,tot,real}}{\sqrt{A_c}} \cdot \log\left(\frac{2G}{l_{g,tot,real}}\right)$$

$$G = 15.45 \text{mm}$$

$$F_{\text{fringe}} = 1.32$$

/ 3 pt.

Q20: ADJUSTMENT OF NUMBER OF TURNS DUE TO FRINGING FLUX

Due to the effect of the fringing field the magnetizing inductance value is modified. While keeping the air gap unchanged (equal to the effective one you obtain using a integer number of Kapton tape layers - Q18), recalculate the number of turns needed to obtain your desired L_m . Calculate $N_{1,new}$ and adjust the the number of turns of the primary to obtain the desired transformer ratio. Also in this case, make sure that each winding is composed by a discrete number of turns.

We have $R_{g,new} = \frac{l_{g,tot,real}}{\mu_0 \cdot A_c} = \frac{0.58 \cdot 10^{-3} \text{ m}}{4\pi \cdot 10^{-7} \cdot 0.52 \cdot 10^{-4}}$ which leads us to find $N_{1,new} = \sqrt{R_{g,new} \cdot L_m}$ and $N_{2,new} = \frac{N_{1,new}}{n}$

$$N_{1,new} = 13$$

$$N_{21,new} = 12$$

$$N_{22,new} = 12$$

/ 3 pt.

Q21: CHECK ON MAXIMUM FLUX

Using the inverse of the formula you applied in Q11. Calculate the maximum ΔB expected with the newly selected number of turns. Check that this is still below the $B_{pk,max}$ you selected in Q1 to avoid saturation.

$$\Delta B_{new} = \frac{\lambda}{2 \cdot N_{1,new} \cdot A_c} \cdot 10^4 = 128 \text{ mT} < B_{pk,max}$$

$$\Delta B_{new} = 0.128 \text{ T}$$

/ 3 pt.

Q22: EVALUATION OF EXPECTED MAGNETIZING INDUCTANCE VALUE

Compute the final value of the magnetizing inductance using the new number of turns just select. You can use the inverse of the formula you used to compute the number of turns.

$$L_{m,final} = \frac{N_{1,new}^2}{R_{g,new}}$$

$$L_{m,final} = 18.87 \mu\text{H}$$

/ 3 pt.

VERIFICATION OF THE DESIGN CONSTRAINTS AND EVALUATION OF LOSSES

Q23: WINDOW UTILIZATION FACTOR

Considering the core and wires you selected, calculate the current window utilization factor $K_{u,real}$ to verify if the core window area is too occupied, before coming to the practical winding. Compare it with your initial estimate in Q5.

$$K_{u,real} = \frac{N_{1,new} \cdot A_{w1,selected} + 2 \cdot N_{2,new} \cdot A_{w2,selected}}{W_a}$$

$$K_{u,real} = 0.29$$

/ 2 pt.

Q24: DC WINDING RESISTANCE

Calculate the DC winding resistance R_L of the designed transformer. Use thereby the MLT (from core datasheet), A_w (from selected wires, use total conductive area) and the resistance per length for copper wire ($\rho = 1.724e - 6\Omega cm$).

From the Datasheet we get MLT = 4.9cm so:

$$R_{L1} = \frac{\rho \cdot N_{1,new} \cdot MLT}{A_{w1,selected}} \quad , \quad R_{L2} = \frac{\rho \cdot N_{2,new} \cdot MLT}{A_{w2,selected}}$$

$$R_{L1} = 0.017\Omega$$

$$R_{L21} = 0.0305\Omega$$

$$R_{L22} = 0.0305\Omega$$

/ 3 pt.

Q25: AC WINDING RESISTANCE

Calculate the AC winding resistance $R_{L,ac}$ only taking into account skin depth, you are allowed to neglect proximity effect and other phenomena. **Note:** skin effect is only effecting your resistance if the radius of each of your isolated conductors is bigger than your skin depth.

$$R_{L1,ac} = \frac{0.9}{2} \cdot \frac{R_{L1}}{2 \cdot \delta_{f,max}} \quad , \quad R_{L2,ac} = \frac{0.65}{2} \cdot \frac{R_{L2}}{2 \cdot \delta_{f,max}}$$

$$R_{L1,ac} = 0.0235\Omega$$

$$R_{L21,ac} = 0.03\Omega$$

$$R_{L22,ac} = 0.03\Omega$$

/ 4 pt.

Q26: DC E AC COPPER LOSSES

Calculate the total DC copper losses $P_{Cu,dc}$ and AC copper losses $P_{Cu,ac}$, which arise due to the currents flowing through all the windings of the transformer. Perform calculation considering nominal power, both at minimum and maximum input voltage. Calculate the percentage of the nominal output power to which the AC copper losses correspond to.

We begin by calculating $R_{L1,ac,min} = \frac{0.9}{2} \cdot \frac{R_{L1}}{2 \cdot \delta_{f,min}}$ and $R_{L2,ac,min} = \frac{0.65}{2} \cdot \frac{R_{L2}}{2 \cdot \delta_{f,min}}$. We then find:

$$P_{Cu,dc,min} = R_{L1} \cdot I_1^2 + 2 \cdot R_{L2} \cdot I_2^2 \quad , \quad P_{Cu,ac,min} = R_{L1,ac,min} \cdot I_1^2 + 2 \cdot R_{L2,ac,min} \cdot I_2^2$$

and

$$P_{Cu,dc,max} = R_{L1} \cdot I_1^2 + 2 \cdot R_{L2} \cdot I_2^2 \quad , \quad P_{Cu,ac,max} = R_{L1,ac} \cdot I_1^2 + 2 \cdot R_{L2,ac} \cdot I_2^2$$

With minimum input voltage: $P_{Cu,dc} = 0.39 \text{ W}$ and $P_{Cu,ac} = 0.38 \text{ W}$ which corresponds to 1.54 % of the output power.

With maximum input voltage: $P_{Cu,dc} = 0.39 \text{ W}$ and $P_{Cu,ac} = 0.45 \text{ W}$ which corresponds to 1.68 % of the output power.

/ 3 pt.

Q27: ESTIMATION OF CORE LOSSES

With the help of a core loss density plot provided in the material's data sheet (N87), estimate the core losses P_{core} of the designed transformer. The core volume can be instead found in the core shapes databook (Ferroxcube). Calculate the percentage of the nominal output power to which the core losses correspond to.

From the datasheet, we find the effective volume $V_e = 2990mm^3$ and $P_v = 110kW/m^3$. We then find:

$$P_{core} = P_v \cdot V_e \cdot 10^{-9} \cdot 10^3$$

$P_{core} = 0.33 \text{ W}$ which corresponds to 0.66% of the output power.

/ 3 pt.

Q28: THERMAL CONSIDERATION

For the worst operating condition, calculate the total losses (copper plus core) expected in your transformer and compare them with the loss budget you defined in Q6. Estimate the temperature rise of the designed transformer. You can find values for the thermal resistance R_{th} and the temperature rise limit of different materials in the TDK EPCOS databook on the pages 161 and 168. Make sure the temperature rise you estimate is allowable for the material. If this is not the case review your core and wire selection.

$$P_{tot} = P_{core} + P_{Cu,dc,max} + P_{Cu,ac,max} = 0.3289W + 0.3977W + 0.452W = 1.18$$

$$\Delta T = R_{th} \cdot P_{tot} = 40K/W \cdot 1.18W = 47.2K < 50K$$

From the datasheet, we get that the temperature rise limit for the N87 material is $\Delta T = 50K$ so our temperature rise = $47.2K$ is allowable for the material.

$P_{tot} = 1.18W$

$\Delta T = 47.2K$

/ 3 pt.

TRANSFORMER DESIGN SUMMARY

Q29: LLC TRANSFORMER DESIGN

Fill Table 5 given below with your design results. Do not forget to include the units.

Table 5 LLC transformer design summary

Electrical specification		
Desired Magnetizing inductance	L_m^*	18.25 μ H
Designed Magnetizing inductance	L_m	18.87 μ H
Primary current	$I_{L,w1,rms}$	3.05 A
Secondary current	$I_{L,w2,rms}$	1.97 A
Operating frequency range	$f_{sw,min} - f_{sw,max}$	[115.25, 160] kHz
Core specification		
Core shape and size		E25/13/7
Coil former		B66208X1010T001
Core material		N87
Max flux density	ΔB	128mT
Total Air gap length	l_g	0.585mm
Number of Kapton tape layers per side	N_{layers}	9
Winding specification		
wire 1 diameter	\varnothing	0.9mm
number of turns for wire 1	N	13
wire 2,1 diameter	\varnothing	0.65mm
number of turns for wire 2,1	N	12
wire 2,2 diameter	\varnothing	0.65mm
number of turns for wire 2,2	N	12
Losses and temperature rise		
Core losses	P_{core}	0.33W
DC Winding losses	$P_{Cu,dc}$	0.39W
Total inductor losses	$P_{L,loss}/P_{out}$	2.34 %
Expected Temperature rise	ΔT	47.14K K

/ 1 pt.

Q30: OVERALL EFFICIENCY OF THE LLC CONVERTER

Taking into account the results of the Loss Tool of Report 1, estimate the best-case and the worst-case overall efficiency of your LLC converter for the nominal output power considering the transformer losses estimated theoretically (Q26 and Q27).

We know that $P_{loss,vmin} = P_{losscopper,vmin} + P_{losscore,vmin} = 0.39 + 0.38 + 0.33 = 1.1W$ and

$$P_{loss,vmax} = P_{losscopper,vmax} + P_{losscore,vmax} = 0.39 + 0.45 + 0.33 = 1.17W$$

which gives us:

$$\eta_{LLC,best} = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{loss,vmin}} = \frac{50W}{50W + 1.1W} = 0.978$$

$$\eta_{LLC,worst} = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{loss,vmax}} = \frac{50W}{50W + 1.18W} = 0.977$$

$$\eta_{LLC,best} = 97.8 \%$$

$$\eta_{LLC,worst} = 97.7 \%$$

/ 3 pt.

TRANSFORMER BUILDING PROCEDURE

Q31: WIRING OF THE TRANSFORMER

Based on the theoretical calculations done above, choose:

- 1x Coil former !! **Careful: Pins are easy to bend and break! The main structure is made of plastic, don't push the clamp to hard it can break**
- 2x Core halves !! **Careful: Very fragile! Do not drop !!**
- 2x Yoke

Proceed with these items to the assembly station where you use the coil former to start wiring your transformer. Wind the appropriate number of turns for your primary and your two secondaries (Q20), using the appropriate wire according to your choices (Q16). It is strongly suggested to interleave the tree winding, especially if your desired resonance (and therefore leakage) inductance is very low ($\leq 2\mu H$), this means wiring all your three windings at the same time. If you can allow a big leakage inductance you can consider wire one winding at a time and try different disposition of primary and secondary. **Note:** leave some margin (ca. 4-6 cm) at the end of each side of the windings to make following steps easier. **Note:** Mark differently the beginning and end of each of your windings to help connecting them appropriately.

Add a picture after the last step of the above mentioned assembly process.

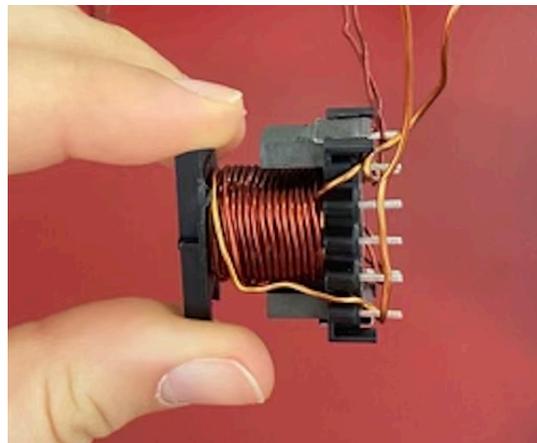


Figure 2 Transformer after the winding.

/ 2 pt.

Q32: AIR GAP AND ASSEMBLY OF THE TRANSFORMER

Following the wiring of your transformer, proceed with:

- Inserting a single core half into the coil former
- Adding the right amount of Kapton tape layers on the two external legs
- Inserting the second core half into the other side of the coil former
- Use the yokes to hold the transformer together

Note: it can require quite a bit of force to install the yokes, use the provided tools and be careful to not break the cores.

Add a picture after the last step of the above mentioned assembly process.

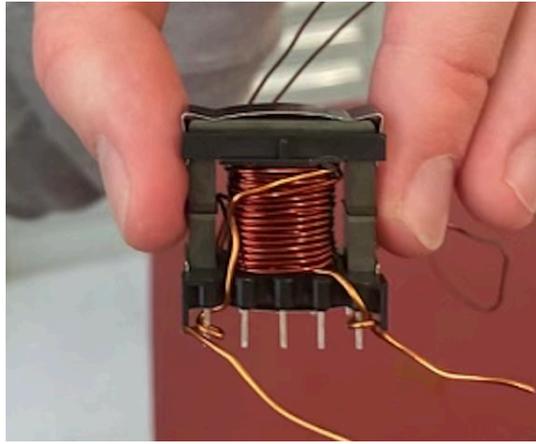


Figure 3 Transformer with its enclosure and the Kapton tape.

/ 2 pt.

Q33: VERIFYING THE WIRING DIRECTIONS

Using the RLC meter as a supply connected to the terminals of the primary winding, verify the winding direction of the secondaries winding by following the steps below:

- Set the frequency on the RLC to 10kHz
- Mark the terminal of the primary winding connected to the high potential of the RLC
- Measure the voltage across the secondary windings
- If the voltage is in phase with the primary voltage, mark the positive terminal, otherwise mark the negative terminal

Provide a picture of the inductor with the markings on the three windings.

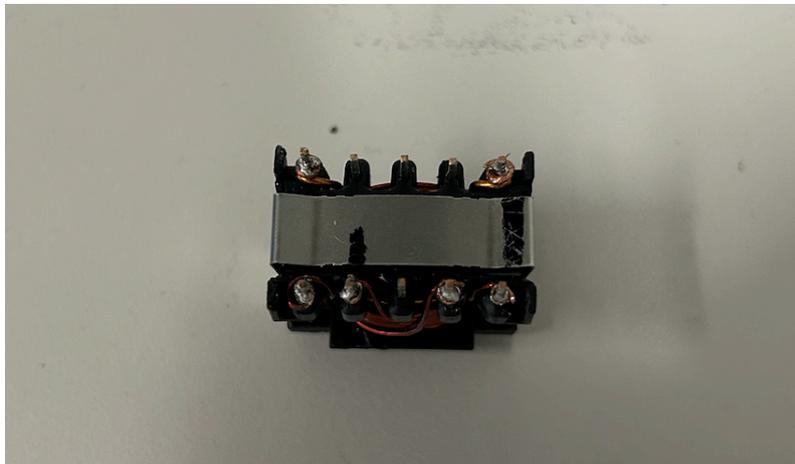



Figure 4 Inductor with the markings on the three windings.

/ 2 pt.

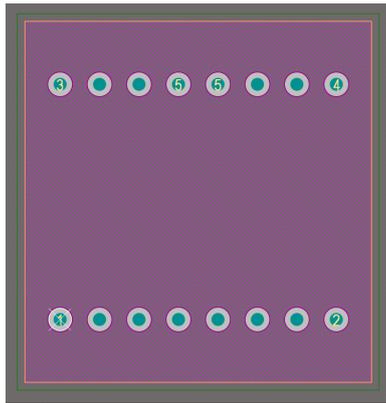Q34: SOLDERING

Solder the windings to the respective pins of the coil former and provide a picture of the final soldered transformer. **Note:** Make sure to solder the winding terminals to the right pins **Note:** You need to remove isolation from the wires before soldering. If you are using bare wire you can scratch the varnish with sandpaper or camps' or scissors' blades. If you are using Litz wires you need to terminate them using soldering bath (keep the wire inside the bath for 10-20 seconds according to the size of your wire)

Add a picture after completing the soldering process.



(a) Footprint



(b) Coilformer

Figure 5 Transformer suggested connection: Solder the beginning of your primary to pin 1, the its end to 2; Solder the beginning of your first secondary to pin 3, and its end to pin 5(3); Solder the beginning of your second secondary to pin 5(4), and its termination to pin 4

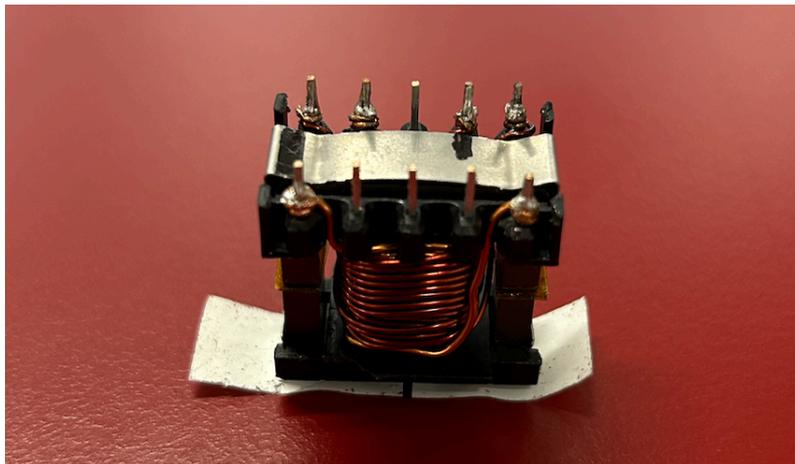


Figure 6 Transformer with its wires soldered to their pins.

/ 2 pt.

TRANSFORMER MEASURING PROCEDURE

Q35: OPEN CIRCUIT TEST WITH RLC METER

Measure your magnetizing inductance using the RLC Meter. Keep both secondaries winding open and measure the inductance (L_s mode) on the primary winding. Repeat the measurements for your minimum, nominal and maximum frequency. Show a picture of your measurement set up. Compare this value with your desired magnetizing inductance. If the value is not matching review your design and building procedure. If needed, one non invasive first attempt solution could be to modify the number of Kapton layers.

We get a magnetizing inductance $L_m \approx 15.5\mu H$ which corresponds to 82% of the final expected magnetizing inductance ($L_{m,final} = 18.87\mu H$) and 85% of our originally calculated magnetizing inductance ($L_m = 18.25\mu H$). For both cases, it is in the 20% margin, so we can keep this value for our transformer.



Figure 7 Magnetizing inductance measurement set up.

$L_m = 15.57\mu H$	at	$f_{min} = 115.25$ kHz
$L_m = 15.55\mu H$	at	$f_{nom} = 133.9$ kHz
$L_m = 15.52\mu H$	at	$f_{max} = 160$ kHz

/ 3 pt.

Q36: SHORT CIRCUIT TEST WITH RLC METER

Measure your leakage inductance and resistance using the RLC Meter. Short circuit both secondaries winding using wire or clips, and measure the inductance and resistance (L_s-R_s mode) on the primary winding. Repeat the measurements for your minimum, nominal and maximum frequency. Show a picture of your measurement set up. Compare the inductance value with your desired resonance inductance and make sure that your leakage inductance is smaller than the resonant inductor value that you need. If the constraint is not fulfilled rewind your transformer. Then compare your expected resistance measured with the one you estimated in Q25. **Note:** The value you measure is the series of your primary side resistance plus the parallel of the resistance of your secondary windings reflected to primary side. Notice the effect of frequency on your resistance.

The leakage inductance we get is well below the resonant inductor value that we need ($0.48\mu H \ll 3.65\mu H$). We can see that the resistance increases with the frequency. In Q25, we estimated the resistance to be: $R_{tot} = R_{L1} + \frac{R_{L21} \cdot R_{L22}}{R_{L21} + R_{L22}} = 0.0405 + \frac{0.06^2}{0.06 + 0.06} = 0.07\Omega$. This result is a lot smaller than the one we measured, as our calculations would match a perfect winding and doesn't estimate potential loss in the wire/soldering.

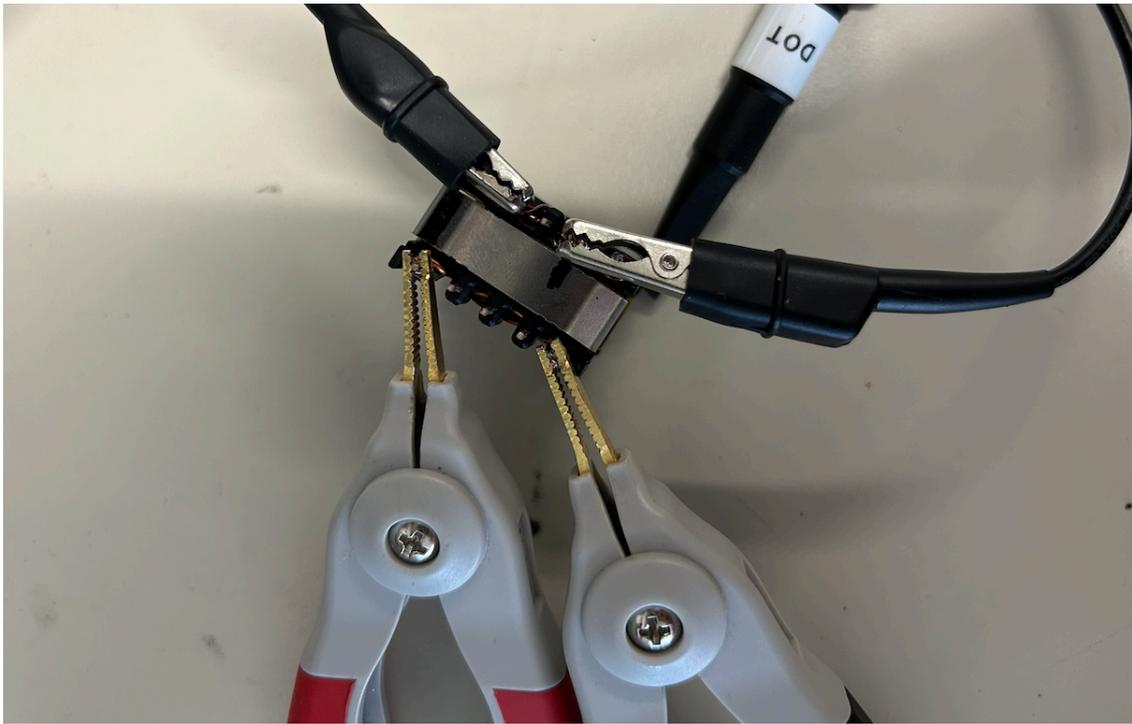


Figure 8 Leakage inductance and resistance measurement set up.

$L_{leak} = 0.48\mu H$	$R_s = 0.26\Omega$	at	$f_{min} = 115.25kHz$
------------------------	--------------------	----	-----------------------

$L_{leak} = 0.39\mu H$	$R_s = 0.27\Omega$	at	$f_{nom} = 133.9kHz$
------------------------	--------------------	----	----------------------


$L_{leak} = 0.36\mu H$	$R_s = 0.30\Omega$	at	$f_{max} = 160kHz$
------------------------	--------------------	----	--------------------

/ 4 pt.

Q37: OPEN CIRCUIT TEST WITH BODE 100 METER

Validate the measurements you took in Q35 using the Bode 100 Meter. Keep both secondary windings open and measure the inductance (Impedance Analysis/One-Port/Ls) on the primary winding. Provide a screenshot showing the measured inductance for a frequency range from 100 Hz to 1 MHz.

Measurement: One-Port

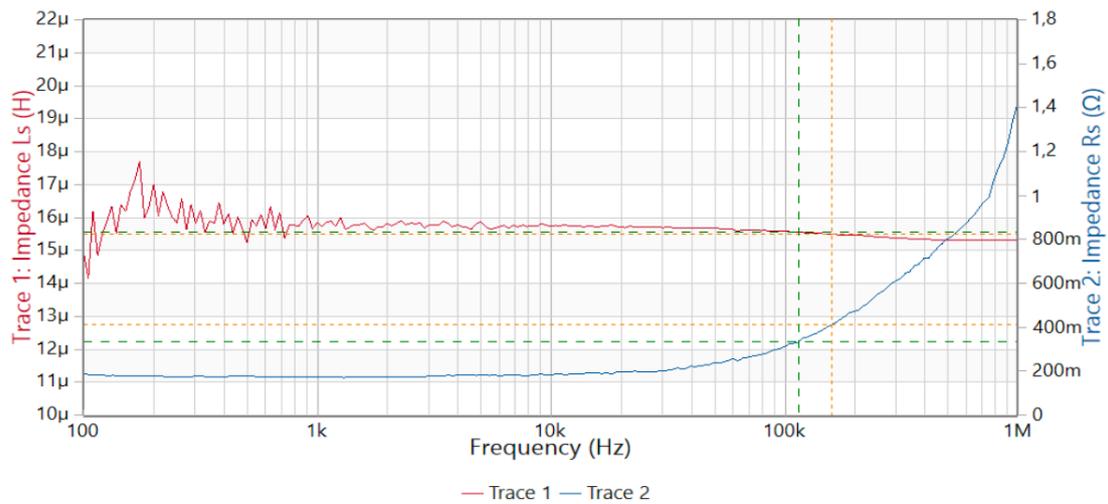

	Cursor 1	Cursor 2	Delta C2-C1
Frequency	115,25 kHz	160 kHz	44,75 kHz
Trace 1	Ls	Ls	Ls
Measurement	15,554 μH	15,494 μH	-60,699 nH
Trace 2	Rs	Rs	Rs
Measurement	332,87 mΩ	412,445 mΩ	79,575 mΩ

Sweep

Start frequency:	100 Hz
Stop frequency:	1 MHz
Center frequency:	500,05 kHz
Span:	999,9 kHz
Sweep mode:	Logarithmic
Numer of points:	201

Calibration

Impedance	Full-Range	User-Range
	Active	-

Attenuator setting

Reflection	Channel 1	Channel 2
	10 dB	10 dB

Hardware setup


Device type:	Bode100R1
Serial number:	ML700D
Receiver bandwidth:	300 Hz
Output level:	0 dBm
DUT settling time:	0 s

/ 3 pt.

Q38: SHORT CIRCUIT TEST WITH BODE 100 METER

Validate the measurements you took in Q36 using the Bode 100 Meter. Short Circuit both secondary winding and measure the inductance and resistance (Impedance Analysis/One-Port/Ls+Rs) on the primary winding. Provide a screenshot showing both the measured inductance and the measured resistance for a frequency range from 100 Hz to 1 MHz.

Measurement: One-Port

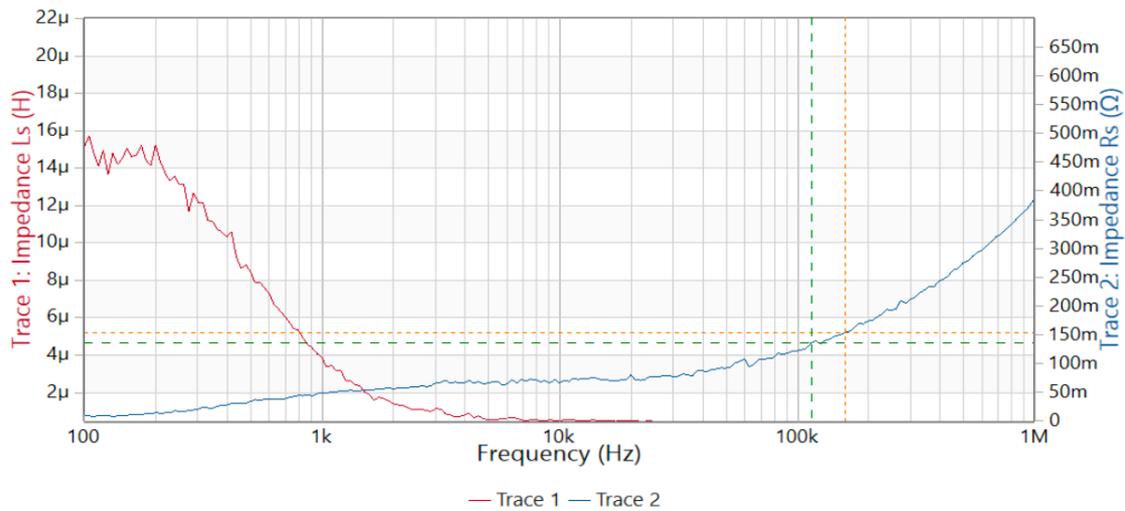

	Cursor 1	Cursor 2	Delta C2-C1
Frequency	115,25 kHz	160 kHz	44,75 kHz
Trace 1	Ls	Ls	Ls
Measurement	356,273 nH	328,879 nH	-27,394 nH
Trace 2	Rs	Rs	Rs
Measurement	135,857 mΩ	153,823 mΩ	17,966 mΩ

Sweep	
Start frequency:	100 Hz
Stop frequency:	1 MHz
Center frequency:	500,05 kHz
Span:	999,9 kHz
Sweep mode:	Logarithmic
Number of points:	201

Calibration	Full-Range	User-Range
Impedance	Active	-

Attenuator setting	Channel 1	Channel 2
Reflection	10 dB	10 dB

Hardware setup	
Device type:	Bode100R1
Serial number:	ML700D
Receiver bandwidth:	300 Hz
Output level:	0 dBm
DUT settling time:	0 s

/ 3 pt.

Q39: SATURATION MEASUREMENTS

Using the power choke meter, execute the saturation test and provide the results below.

- Keep the secondary windings open
- Connect both the Force and Sense cable to the power choke meter and to the terminals of the primary inductance
- Once connected, cover with Plexiglas box and do not touch until the end of the measuring process

Software settings:

- The max current value corresponds to your maximum input current rounded up
- The measured voltage value corresponds to your maximum input voltage
- For the pulse time enter 10ms

Verify that your core is not saturating and provide the curve of both the incremental and the secant inductance below as well as a picture of the measuring setup.

In Figure 10 we see that our core is saturating around 15A and our max current is < 10A so we have a lot of safe margin.


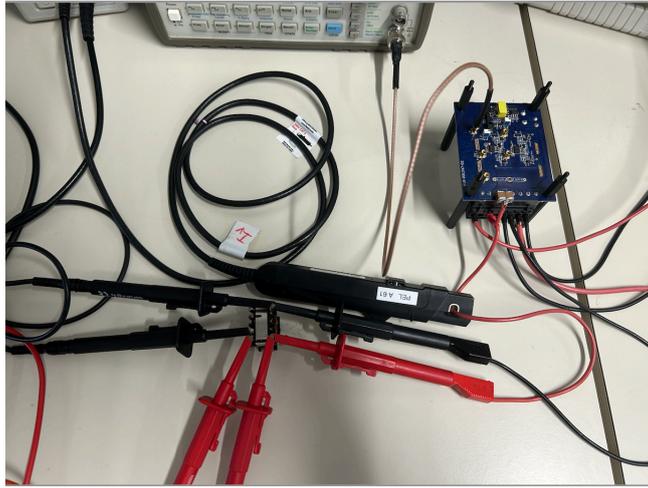


Figure 9 Setup for the Power Choke test.

DPG10 Power Choke Tester

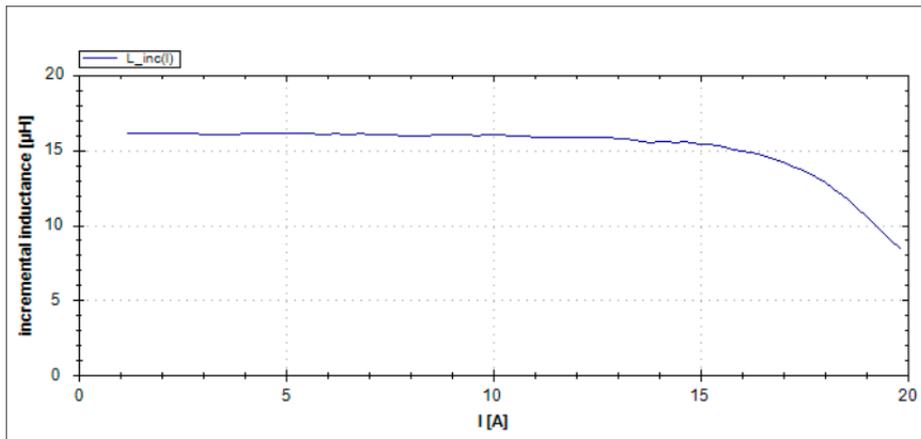D.U.T.: group5_20A
 Inspector:
 Date: 09.04.2024 10:22:14
 Parameters: 20 A / 15 V / 30 (32) μ s
 Resistance [Ohm]: 0,0184



Current [A]	L _{inc} [μH]								
		4,2	16,1	8,2	16,0	12,2	15,9	16,2	14,9
		4,4	16,1	8,4	16,0	12,4	15,8	16,4	14,7
		4,6	16,1	8,6	16,0	12,6	15,8	16,6	14,6
		4,8	16,1	8,8	16,0	12,8	15,8	16,8	14,4
		5,0	16,1	9,0	16,0	13,0	15,8	17,0	14,2
1,2	16,1	5,2	16,1	9,2	16,0	13,2	15,7	17,2	14,0
1,4	16,1	5,4	16,1	9,4	16,1	13,4	15,7	17,4	13,7
1,6	16,1	5,6	16,1	9,6	16,0	13,6	15,6	17,6	13,5
1,8	16,1	5,8	16,1	9,8	16,0	13,8	15,5	17,8	13,2
2,0	16,1	6,0	16,1	10,0	16,0	14,0	15,6	18,0	12,8
2,2	16,1	6,2	16,1	10,2	16,0	14,2	15,5	18,2	12,4
2,4	16,1	6,4	16,1	10,4	15,9	14,4	15,5	18,4	12,0
2,6	16,1	6,6	16,0	10,6	15,9	14,6	15,6	18,6	11,5
2,8	16,1	6,8	16,1	10,8	15,9	14,8	15,5	18,8	11,0
3,0	16,0	7,0	16,1	11,0	15,9	15,0	15,4	19,0	10,5
3,2	16,1	7,2	16,0	11,2	15,9	15,2	15,4	19,2	9,99
3,4	16,1	7,4	16,0	11,4	15,9	15,4	15,3	19,4	9,47
3,6	16,1	7,6	16,0	11,6	15,8	15,6	15,2	19,6	8,92
3,8	16,1	7,8	16,0	11,8	15,9	15,8	15,1	19,8	8,42
4,0	16,1	8,0	16,0	12,0	15,9	16,0	15,0		

Figure 10 Result of the Power Choke test.

Q40: MAGNETIZING CURRENT AND VOLTAGE RATIO CHECK

Using the provided hardware setup excite your transformer to your maximum and minimum frequency.

- Use DC power supply to provide auxiliary power to the Half Bridge (5V)
- Use DC power supply to input power to the Half Bridge (45V)
- Use Tektronix function generator to provide the switching signal to the half bridge (square-wave with amplitude 5Vpp)
- Connect your the output of the Half Bridge to the primary of your transformer

For your minimum and maximum frequencies report the oscilloscope acquisition of primary voltage, secondary voltages and magnetizing current.

From our PLEX simulation, we get 1.57593A for f_{min} and 1.23588A for f_{max} which matches quite well the values we get in Figure 11 & 12 (1.5A for f_{min} and 1.4A for f_{max}).



Figure 11 Acquisition of primary voltage, secondary voltages and magnetizing current at minimum frequency.

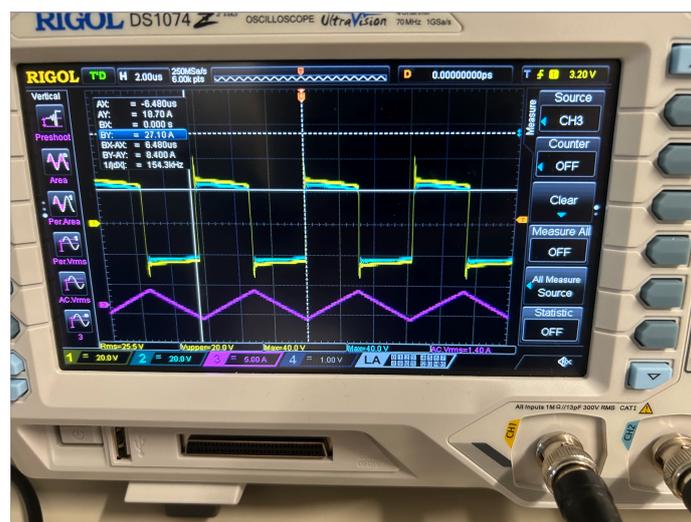


Figure 12 Acquisition of primary voltage, secondary voltages and magnetizing current at maximum frequency.

Q41: HEAT-RUN TEST

Using the set up provided for previous question, execute a heat-run test. Provide a picture of the test-setup as well as two thermal images, one done prior to the test and one after 15 minutes of test.



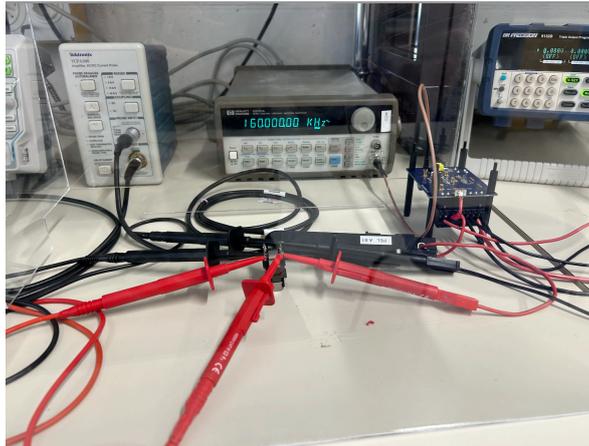


Figure 13 Setup for the Heat-Run test.

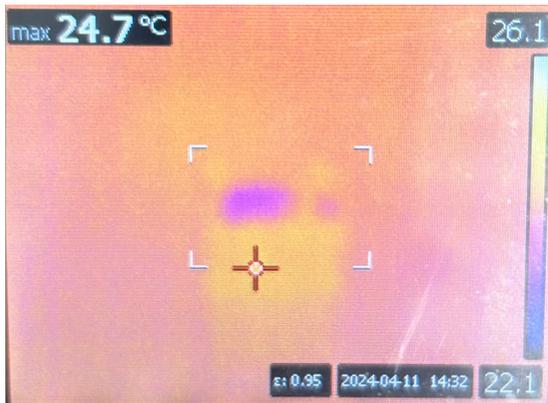

(a) Before the test

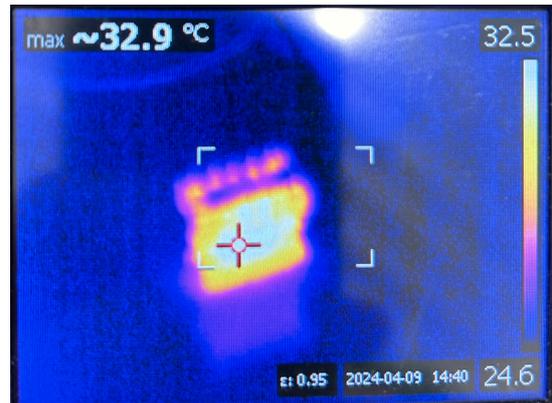

(b) After 15 minutes of test

Figure 14 Thermal images of the transformer before 14a and after 14b the Heat-Run test.

$$T_{init} = 25^{\circ}C$$

$$T_{final} = 32^{\circ}C$$

/ 3 pt.

DESIGN OF THE RESONANT INDUCTOR

The aim of this last section is to design and build your external inductor to integrate your leakage inductance and reach the desired value for your resonant inductance. This process is also iterative, please be aware that you could need to reconsider your choices. Questions of this section represent an independent iterative loop with respect to the previous (it is only influenced by the measured leakage inductance Q36 and Q38). Your inductor will be built winding one wire (choose the same wire you used for the primary side of your transformer) around one toroidal core. Be aware that it may not be possible to realize exactly the value of your choice, small deviation can be expected, they may be compensated when choosing your resonant capacitor in Report 3 or simply tolerated.

Q42: EVALUATE THE EXTERNAL INDUCTANCE

Based on the measured leakage inductance (Q36 validate in Q38), and on the desired L_r , calculate the external inductance you need to add in order to reach the desired inductance value.

$$L_{\text{added}} = L_{r,\text{needed}} - L_{r,\text{measured}} = 3.65\mu\text{H} - 0.48\mu\text{H} = 3.17\mu\text{H}$$

$$L_{\text{added}} = 3.17\mu\text{H}$$

/ 2 pt.

Q43: DESIGN OF THE EXTERNAL INDUCTANCE

Choose one of the core in the Table 6. Evaluate the integer number of turns needed to reach your a value L_s as close as possible to the desired L_{added}

We know that $A_L = \frac{L_r}{N^2}$.

For the core A, $A_L = 7.3 \frac{nH}{N^2}$, so if we were to choose it, we would approximately need: $N^2 = \frac{L_{\text{added}}}{A_L} = \frac{3170nH}{7.3 [nH/N^2]} = 434 \Rightarrow N = 20.83 \approx 21$ turns.

For the core B, $A_L = 24 \frac{nH}{N^2}$ so if we were to choose it, we would approximately need: $N^2 = \frac{L_{\text{added}}}{A_L} = \frac{3170nH}{24 [nH/N^2]} = 132 \Rightarrow N = 11.5 \approx 11$ turns .

In order to have a reasonable number of turns, we first wanted to choose the second core. But our L_s would then have been $L_s = N^2 \cdot A_L = 11^2 \cdot 24 [nH/N^2] = 2904nH = 2.9\mu\text{H}$, which was quite far from the desired L_{added} (with $N = 12$ as well). So we went back to the first core, which gives us $L_s = N^2 \cdot A_L = 21^2 \cdot 7.3 [nH/N^2] = 3.22\mu\text{H} \approx L_{\text{added}}$.

Selected core = B

$$N_{L,s} = 11$$

$$L_s = 3.22\mu\text{H}$$

/ 4 pt.

Table 6 Available toroids

Ref.	Part Number	Material	$A_L [nH/N^2]$	μ_r	Link
A	5968001801	68	7.3	16	Fair-rite 68
B	5967001801	67	24	40	Fair-rite 67

Q44: CHECK FOR B VALUE OF YOUR INDUCTOR

Evaluate the magnetic flux value in your inductor considering your peak primary current and the number of turn you selected in Q43. To limit the losses do not allow it to be higher than 30mT. If you can not fulfill this requirement, try to use the other available core. If this solution is not enough you can parallel two cores, this will have the effect of doubling the core area and therefore halve the inductance

value for the same number of turns. Go back to previous question and recalculate the number of turns. Indicate "2x" in your selected core if you need to use two cores in parallel.

$$F = N \cdot I \quad H = \frac{F}{l_e} \quad B = \mu_0 \mu_r H \quad , \quad [\mu_0] = \frac{H}{m} = \frac{V \cdot \text{sec}}{A \cdot m} \quad , \quad [B] = T = \frac{V \cdot \text{sec}}{m^2}$$

$$B_{L_s, peak} = \mu_0 \mu_r \cdot \frac{N \cdot I}{l_e} = 4\pi \cdot 10^{-7} \text{H/m} \cdot \frac{21 \cdot 10 \text{A}}{5.41 \cdot 10^{-2} \text{m}} = 4.88 \text{mT} < 30 \text{mT}$$

$$B_{L_s, peak} = 4.88 \text{ mT}$$

/ 3 pt.

Q45: WINDING AND MEASUREMENT OF THE INDUCTOR

Using the same wire you selected for your primary transformer wind the calculated number of turns on the selected core. Terminate your wires using the same procedure as for your transformer. Using the RLC meter evaluate L_s and R_s at your minimum and maximum frequency. **Note:** the toroidal cores are also very fragile, manage with caution! **Note:** Distribute your turns evenly around the core to obtain a more similar result to the one calculated theoretically. You can also adjust the position of your turns to tailor your inductor value to the desired one. Once you have fixed the optimal position fix the two winding endings to the core with a small amount of glue or tape (e.g. use the glue gun). Show a picture of your inductor.

Because the spacing between our winding is not very homogeneous, the number of turns we previously calculated isn't very accurate. After testing and refining our design, we established that we actually needed 17 turns. This then gives us an added inductance very close to the one we needed ($L_{added} = 3.17 \mu\text{H}$)

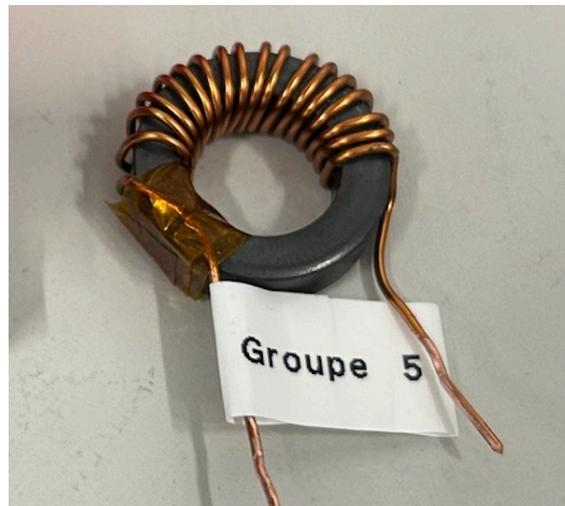


Figure 15 Added Inductor.

$$L_s = 3.18 \mu\text{H} \text{ and } R_s = 0.032 \Omega \text{ at } f_{min} = 115.25 \text{ kHz}$$

$$L_s = 3.18 \mu\text{H} \text{ and } R_s = 0.039 \Omega \text{ at } f_{max} = 160 \text{ kHz}$$

/ 5 pt.

Q46: CHECK EXPECTED COPPER LOSSES IN THE INDUCTOR

Take into account your primary side RMS current and the R_s you measured in Q45 for your maximum frequency. Evaluate the copper losses expected in your inductor and calculate the percentage of the nominal output power to which these losses correspond to. **Note:** It would be advisable not to allow more than 0.5W copper losses in order to avoid heating problems. If this happens it is suggested to change the wire to reduce the resistance (you are eventually allowed to parallel two wires).

$$P_{cu,L} = R_{s,f_{max}} \cdot I^2 = 0.039\Omega \cdot 3.05^2 A = 0.36W < 0.5W$$

$P_{cu,L} = 0.36 W$ which corresponds to 0.72% of output power

/ 2 pt.